

**Circuit #5 Push Buttons**

**1.**

How is this circuit, or a circuit like it, used in everyday life? Provide at least three examples.

---

---

---

---

---

**Can you turn your LED on and off using both buttons?**

Great. Pay attention to this circuit, buttons are one of the most basic forms of user interface.

Give values for Voltage, Current and Resistance for each question. Find Current either by breaking the circuit and/or using your multimeter.

**2.**

**Button on pin 2 pushed:**

$V = \underline{\hspace{1cm}} \text{ v}$   $I = \underline{\hspace{1cm}} \text{ mA}$   $R = \underline{\hspace{1cm}} \Omega$

**3.**

**Button on pin 3 pushed:**

$V = \underline{\hspace{1cm}} \text{ v}$   $I = \underline{\hspace{1cm}} \text{ mA}$   $R = \underline{\hspace{1cm}} \Omega$

**4.**

Think about the question above. What makes the LED turn on and off?

**5.**

If the resistor's value is  $10000\Omega$ , what is the resistance of the button?  $\underline{\hspace{1cm}} \Omega$

**6.**

Replace the LED component (in the space below the schematic to the right) with an element or component from one of the previous circuits. Extra credit if you decide to replace it with a motor.

**7.**

Draw arrows indicating current direction on dotted line.


**8.**

Add another Piezo Element to the schematic so you can write harmonies. Be sure to show which Arduino pin you will attach it to.

**9.**

Add an on/off switch to this schematic.

**Circuit:**

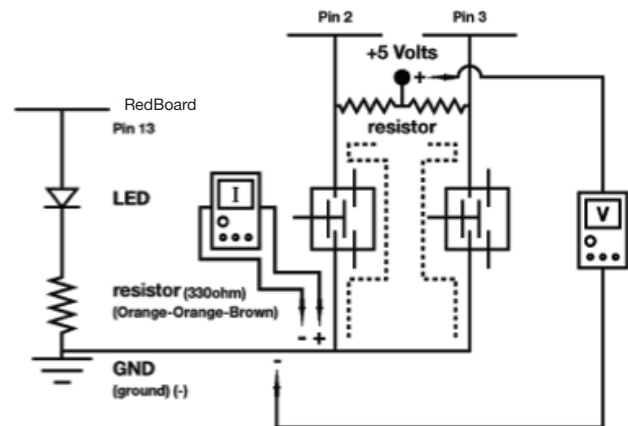



100%

give it a title.